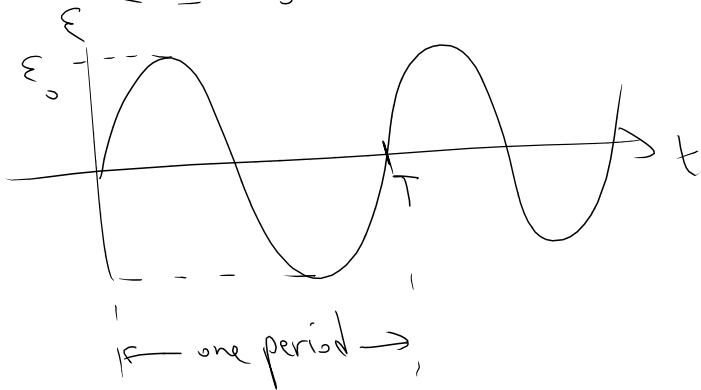


$$v_d \sim 10^{-6} \text{ m/s}$$

$$t \sim \frac{1}{100} \text{ s}$$

$$x = v_d \cdot t \sim 10^{-8} \text{ m}$$


$$\mathcal{E} = \mathcal{E}_0 \cos(\omega t)$$



$$T = \frac{2\pi}{\omega}$$

ω : angular speed

RC

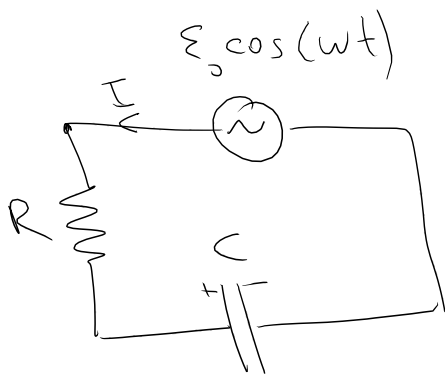

$$\mathcal{E} = \frac{dQ}{dt} = \mathcal{E}_0 \cos(\omega t)$$

$$\mathcal{E} = \frac{dQ}{dt}$$


$$R \frac{dQ}{dt} + \frac{Q}{C} = \mathcal{E}_0 \cos(\omega t)$$

$$Q = Q_0 \cos(\omega t + \delta) = Q_0 \cos \delta \cos \omega t - Q_0 \sin \delta \sin \omega t$$

$$-R\omega \sin(\omega t + \delta) Q_0 + \frac{Q_0}{C} \cos(\omega t + \delta) = \mathcal{E}_0 \cos(\omega t)$$


$$t=0: -\omega R (Q_0 \sin \delta) + \frac{Q_0}{C} \cos \delta = \mathcal{E}_0$$
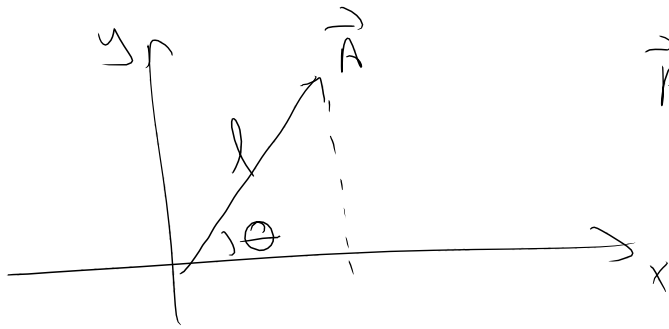
$$\omega t = \frac{\pi}{2}: -\omega R (Q_0 \cos \delta) - \frac{Q_0 \sin \delta}{C} = 0$$



$$\vec{A} = l \cos \theta \hat{x} + l \sin \theta \hat{y}$$

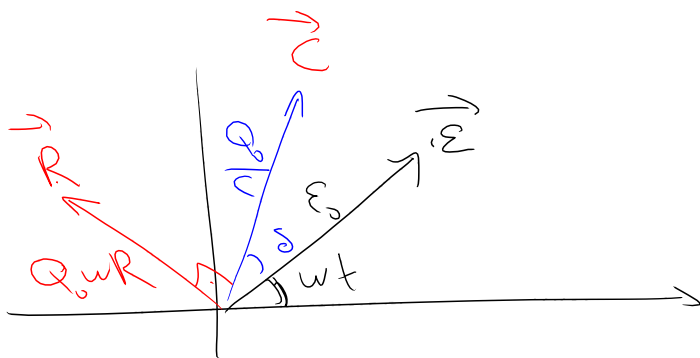
$$-R\omega \sin(\omega t + \delta) Q_0 + \frac{Q_0}{C} \cos(\omega t + \delta) = \varepsilon_0 \cos(\omega t)$$



$$\vec{R} + \vec{C} = \vec{\varepsilon}$$

$$\delta < 0$$
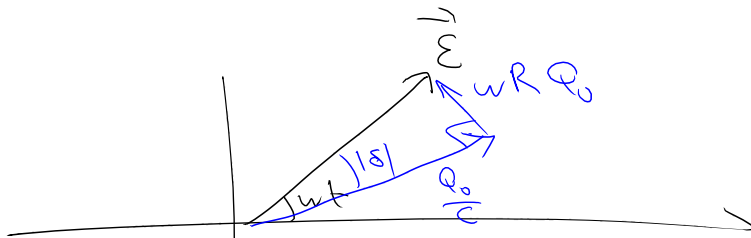
$$-\sin(\omega t + \delta) = \cos(\omega t + \delta + \frac{\pi}{2})$$



"phasor diagram"

$$\varepsilon_0^2 = \left(\frac{Q_0}{C}\right)^2 + (\omega R Q_0)^2 \Rightarrow Q_0^2 \left(\frac{1}{(\omega C)^2} + R^2\right) \omega^2 = \varepsilon_0^2$$


$$Q_0 = \frac{\varepsilon_0}{\omega} \left(R^2 + \frac{1}{(\omega C)^2}\right)^{-1/2}$$

$$\tan |\delta| = \frac{\omega R Q_0}{Q_0/C} = \omega R C$$

$$Q(t) = \frac{\varepsilon_0}{\omega} \frac{1}{\sqrt{R^2 + X_C^2}} \cos(\omega t + \delta)$$

$$I(t) = -\varepsilon_0 \frac{1}{\sqrt{R^2 + X_C^2}} \sin(\omega t + \delta)$$

Example

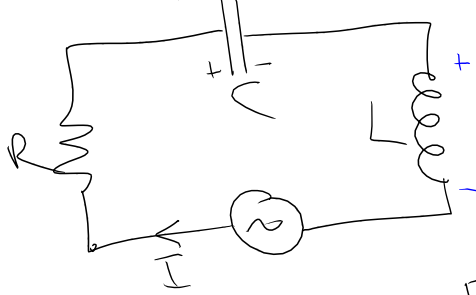

$$IR + \frac{Q}{C} + L \frac{dI}{dt} = \mathcal{E}_0 \sin(\omega t)$$

assume $\frac{dI}{dt} > 0$

$$I = \frac{dQ}{dt}$$

$$\frac{I}{C} + \frac{dI}{dt} R + L \frac{d^2 I}{dt^2} = \omega \mathcal{E}_0 \cos(\omega t)$$

$$kx + \gamma \dot{x} + m \frac{d^2 x}{dt^2} = F$$

forced oscillator with damping

$$I = I_0 \cos(\omega t + \delta)$$

$$\frac{I_0}{C} \cos(\omega t + \delta) - R I_0 \omega \sin(\omega t + \delta) - L \omega^2 I_0 \cos(\omega t + \delta) = \omega \mathcal{E}_0 \cos(\omega t)$$

$$-L \omega I_0 \cos(\omega t + \delta) - R I_0 \sin(\omega t + \delta) + \frac{I_0}{\omega C} \cos(\omega t + \delta) = \mathcal{E}_0 \cos(\omega t)$$

$$X_L = \omega L$$


$$X_C = \frac{1}{\omega C}$$

$$X_R = R$$

$$I_0 \left(-X_L \cos(\omega t + \delta) - X_R \sin(\omega t + \delta) + X_C \cos(\omega t + \delta) \right)$$


$$= \mathcal{E}_0 \cos(\omega t) - X_R \sin(\omega t + \delta)$$
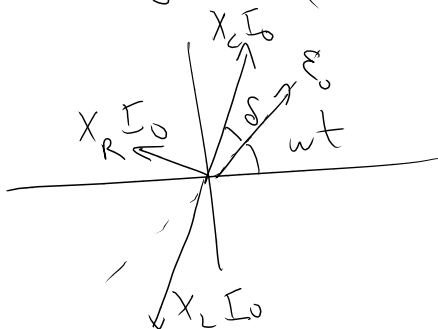
$$= X_R \cos\left(\omega t + \delta + \frac{\pi}{2}\right)$$



$$-L \omega I_0 \cos(\omega t + \delta) - R I_0 \sin(\omega t + \delta) + \frac{I_0}{\omega C} \cos(\omega t + \delta) = \mathcal{E} \cos(\omega t)$$
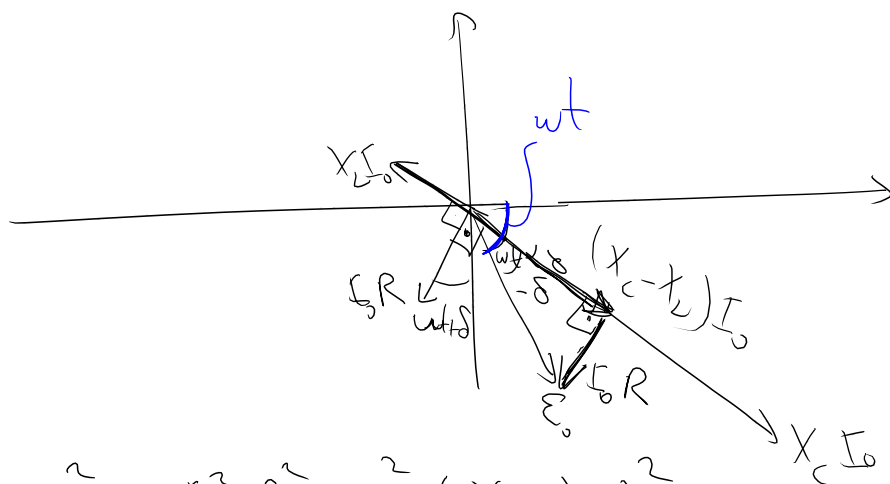
$$L \omega I_0 \sin(\omega t + \delta) - R I_0 \cos(\omega t + \delta) - \frac{I_0}{\omega C} \sin(\omega t + \delta) = -\mathcal{E} \sin(\omega t)$$



$$\mathcal{E}_0^2 = I_0^2 R^2 + I_0^2 (X_C - X_L)^2$$

$$I_0 = \frac{\mathcal{E}_0}{Z} \quad ; \quad Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\tan(-\delta) = \frac{I_0 R}{I_0 (X_C - X_L)} = \frac{R}{X_C - X_L}$$

$$\boxed{\tan \delta = \frac{R}{X_L - X_C}}$$


what happens when $X_L = X_C$?

$$I = I_0 \cos(\omega t + \delta) \iff$$

$$I_0(\omega) = \frac{\mathcal{E}_0}{Z} ; Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\tan \delta = \frac{R}{X_L - X_C}$$


↑
indep
of ω

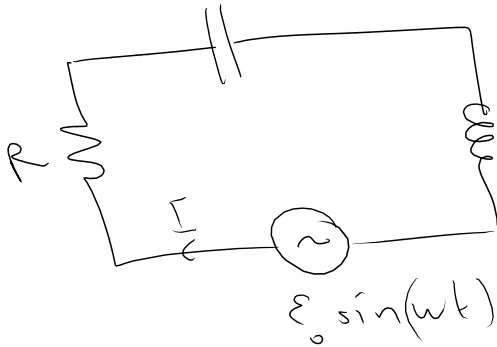

Z is a min when
 $X_C = X_L$: resonance condition

$$\frac{1}{\omega R C} = \omega R L$$
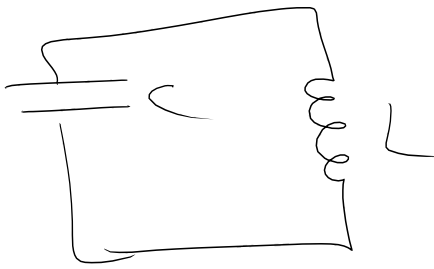
$$\Rightarrow \omega_R = \frac{1}{\sqrt{LC}}$$




$$Q = Q_0 \cos\left(\frac{1}{\sqrt{LC}} t\right)$$

$$\vec{E} = \sum_{\omega} \vec{E}_0(\omega) \cos(\omega t)$$

antenna

$$I_0 \propto$$

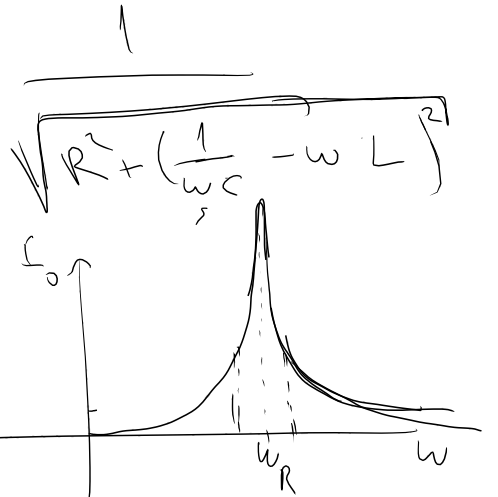


$$I = \sum_{\omega} \frac{(\) E_0(\omega) \cos(\omega t + \delta)}{\sqrt{R^2 + (X_L - X_C)^2}} \approx (\) \frac{E_0(\omega_R) \cos(\omega_R t + \delta)}{R}$$

FM
AM radio


FM: frequency modulation

AM: amplitude modulation.

AM

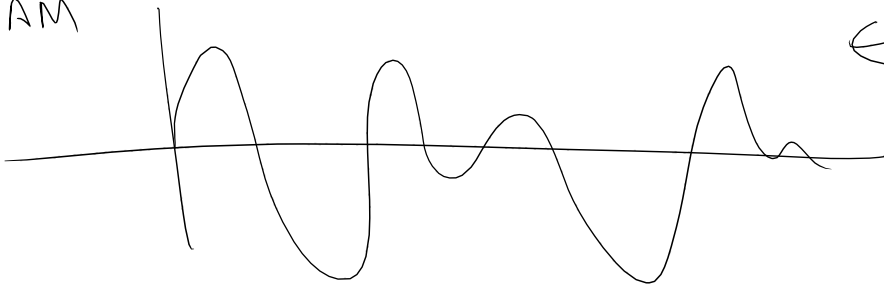


sound signal

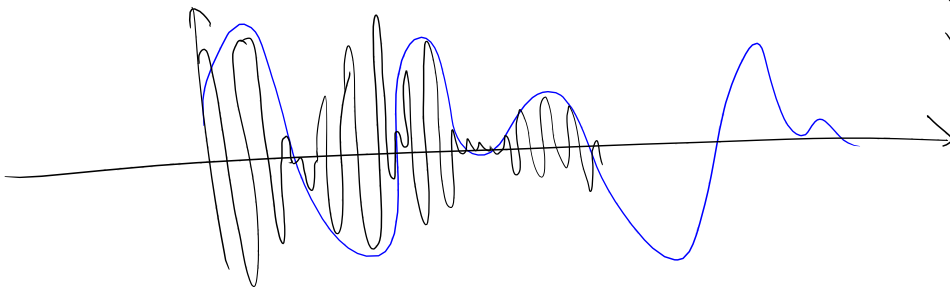

electromagnetic wave of a frequency ω_e


Example

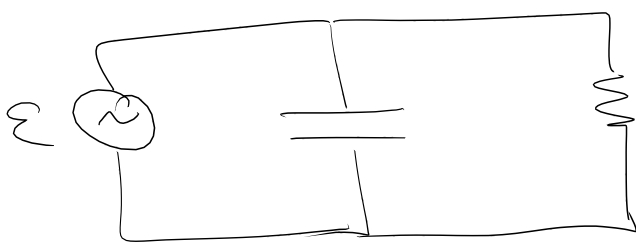


low frequencies will arrive at the resistor.
 high frequencies will not reach the resistor

$$\mathcal{E} = \sum_{\omega} \mathcal{E}(\omega) \cos(\omega t)$$


Low pass filter

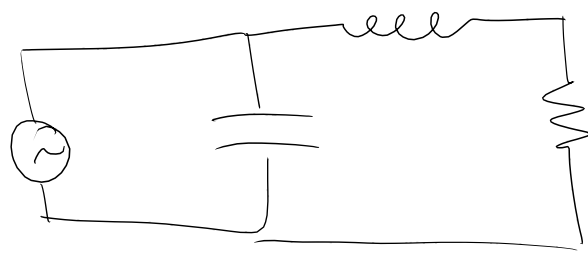

better low pass filter

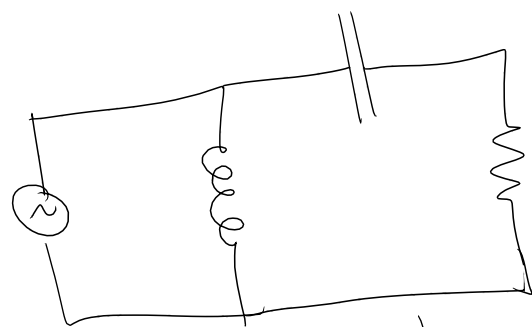

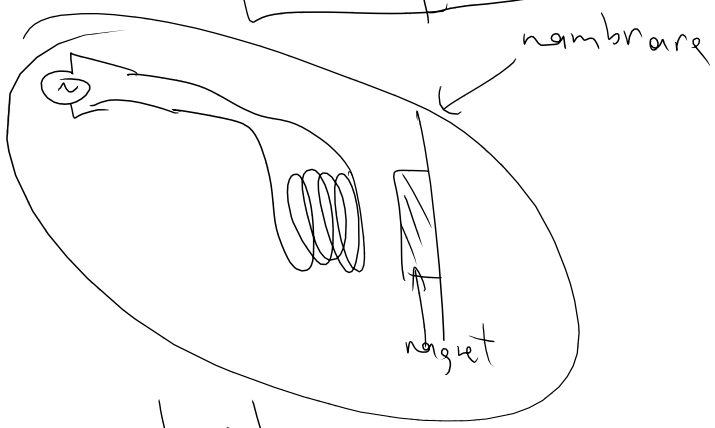low frequencies will not reach the resistor
 high frequencies will reach the resistor
 high pass filter.




Loud speaker

Power

$$P = I^2 R$$

$$I = I_0 \cos(\omega t + \delta)$$
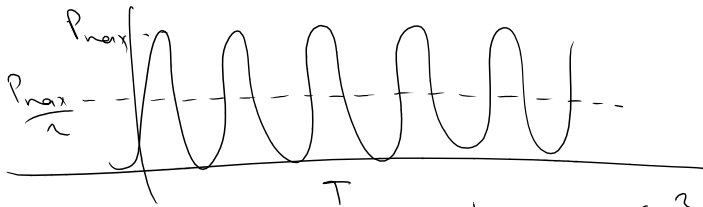
$$P \neq I_0^2 R \cos^2(\omega t + \delta)$$



$$\bar{P} = \frac{1}{T} \int_0^T P(t) dt = \frac{I_0^2 R}{2} = I_{rms}^2 R$$

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

rms : root (of) mean (of) squared

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$f_{rms} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$$

$$\frac{1}{T} \int_0^T \cos^2(\omega t + \delta) dt = \frac{1}{2} \quad ; \quad T = \frac{2\pi}{\omega}$$

$$\bar{P} = I_{rms}^2 R = I_{rms} V_{rms}$$

Power Delivered by the \mathcal{E}

$$P(t) = I \mathcal{E} = I_0 \cos(\omega t + \delta) \mathcal{E}_0 \sin(\omega t)$$


$$\begin{aligned} & \nearrow \\ & = I_0 \mathcal{E}_0 \cos^2(\omega t) \cos \delta - I_0 \mathcal{E}_0 \cos \omega t \sin \omega t \sin \delta \end{aligned}$$

$$\bar{P} = \frac{I_0 \mathcal{E}_0}{2} \cos \delta = I_{rms} \mathcal{E}_{rms} \sin \delta$$

$$\text{if } R = 0 \Rightarrow \sin \delta = 0$$

$$\tan \delta = \frac{R}{X_L - X_C}$$

Transformers (not the optimus prime)

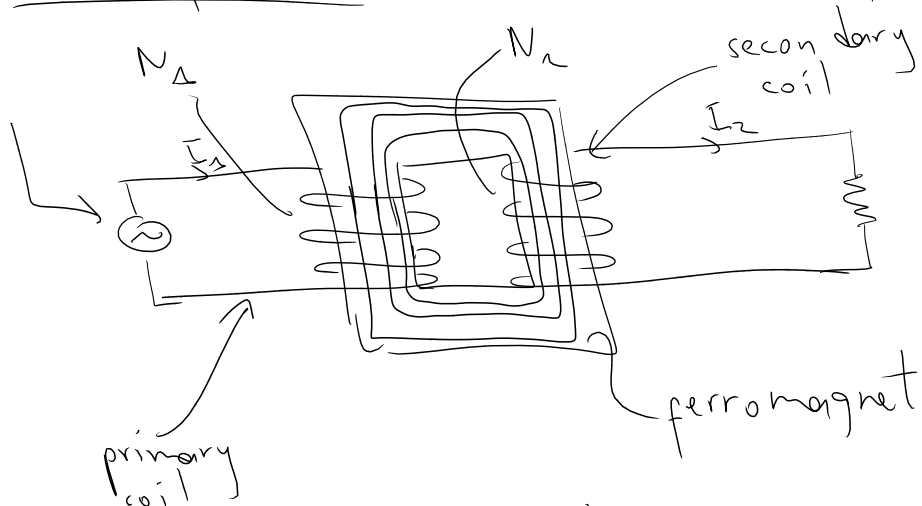

$$E_1 I_1 = E_2 I_2$$

$$P_R = I^2 R$$

ϕ_0 : flux created per ring.

$$\phi_0 = \frac{\phi_1}{N_1} = \frac{\phi_2}{N_2}$$

ϕ_1 : flux through the primary coil

ϕ_2 : flux through the secondary coil.

$$\frac{1}{N_1} \frac{d\phi_1}{dt} = \frac{1}{N_2} \frac{d\phi_2}{dt}$$

$$\frac{E_1}{N_1} = \frac{E_2}{N_2}$$

$$E_2 = \frac{N_2}{N_1} E_1$$

Example
laminated $E_1 = 220\text{ V}$
 $E_2 = 12\text{ V}$

$$\frac{N_2}{N_1} = \frac{12}{220}$$

