

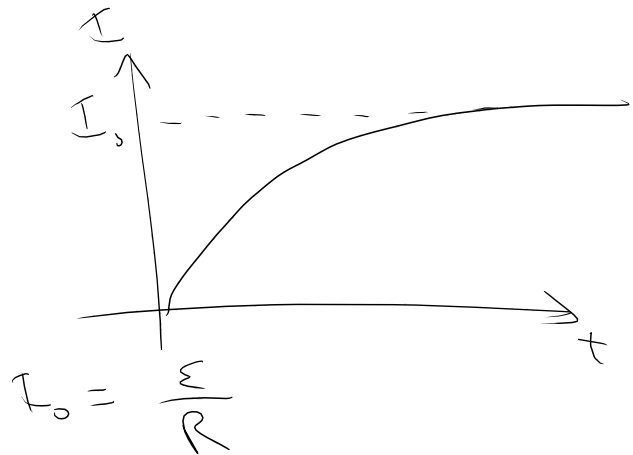


## RL Circuits

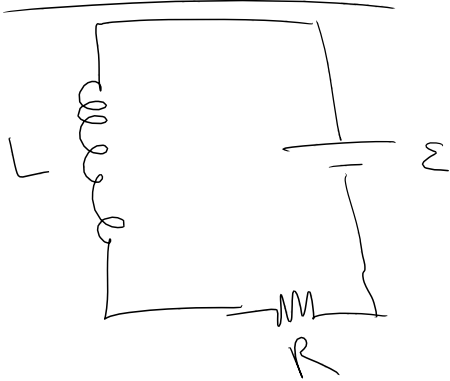


## LC Circuits

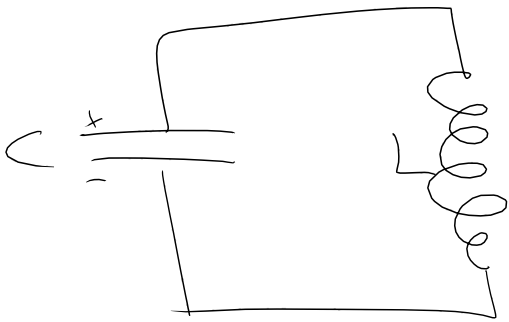

$$Q(t=0) = Q_0$$


$$I(t=0) = 0$$

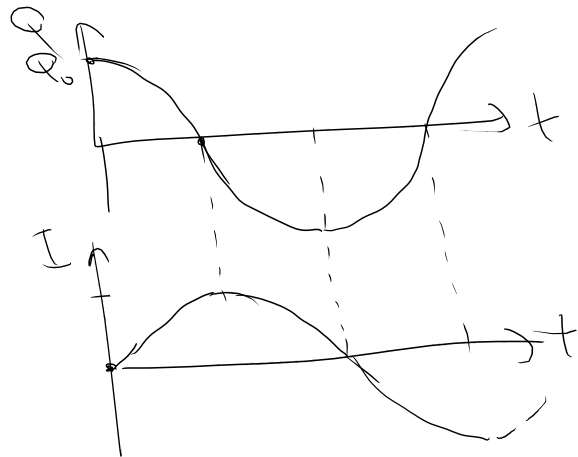

$$I = -\frac{dQ}{dt}$$

"sketch"

## "superconducting cavities"

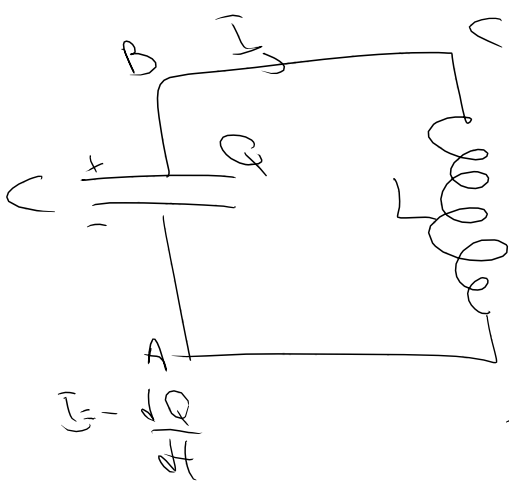

$$-\frac{Q}{C} + L \frac{dI}{dt} = 0$$


assume  $\frac{dI}{dt} > 0$

assume  $\frac{dI}{dt} < 0$

$$\frac{Q}{C} - L \frac{d^2 Q}{dt^2} = 0$$

$$I = \frac{dq}{dt}$$

$$dQ = -dq$$

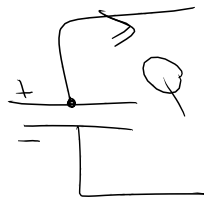

$$\frac{1}{C}Q - L \frac{d^2Q}{dt^2} = 0 \Rightarrow$$

$$\frac{d^2Q}{dt^2} = -\frac{1}{LC}Q$$

$$Q = A \sin(\omega t + \delta)$$

$$\frac{dQ}{dt} = \omega A \cos(\omega t + \delta)$$

$$\frac{d^2Q}{dt^2} = -\omega^2 A \sin(\omega t + \delta) = -\omega^2 Q$$

$$\omega^2 = \frac{1}{LC}$$

$$Q(t) = A \sin\left(\frac{1}{\sqrt{LC}}t + \delta\right) = A \sin\left(\frac{1}{\sqrt{LC}}t\right) \cos \delta + A \cos\left(\frac{1}{\sqrt{LC}}t\right) \sin \delta$$

$$Q(t=0) = Q_0$$

$$A \sin \delta = Q_0$$

$$I(t=0) = 0$$

$$A \cos \delta = 0$$

$$-\frac{dQ}{dt}$$


$$\cos \delta = 0 \Rightarrow \sin \delta = 1$$

$$A = Q_0$$

$$Q(t) = Q_0 \cos\left(\frac{1}{\sqrt{LC}}t\right)$$

Electric pot "exists" if  $\oint \vec{E} \cdot d\vec{l} = 0$

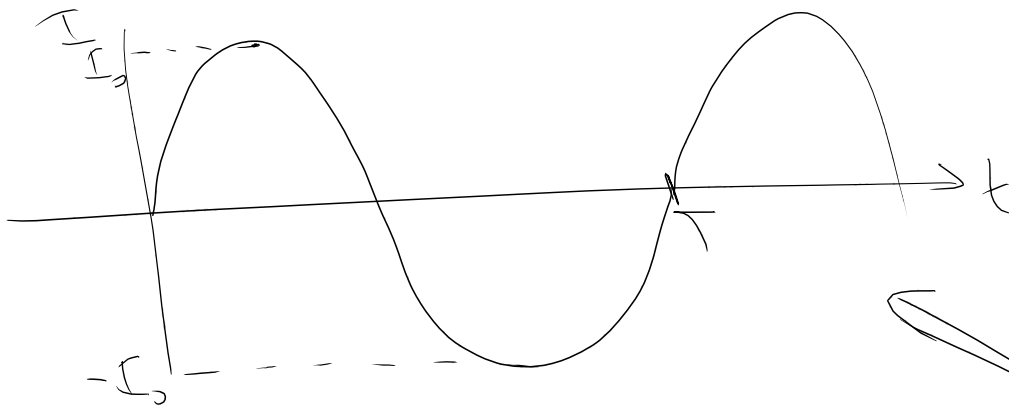BUT  $\oint \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$



Alternating  
Current  
(AC)

$$Q(t) = Q_0 \cos\left(\frac{1}{\sqrt{LC}} t\right)$$

$$I(t) = -\frac{dQ(t)}{dt} = \underbrace{\frac{Q_0}{\sqrt{LC}}}_{I_0} \sin\left(\frac{1}{\sqrt{LC}} t\right)$$


$$T = \frac{2\pi}{\frac{1}{\sqrt{LC}}}$$

$$U_C = \frac{Q^2}{2C} = \frac{Q_0^2}{2C} \cos^2\left(\frac{1}{\sqrt{LC}} t\right)$$

$$U_L = \frac{1}{2} L I^2 = \frac{1}{2} L \frac{Q_0^2}{LC} \sin^2\left(\frac{1}{\sqrt{LC}} t\right)$$

$$U_L = \frac{Q_0^2}{2C} \sin^2\left(\frac{1}{\sqrt{LC}} t\right)$$
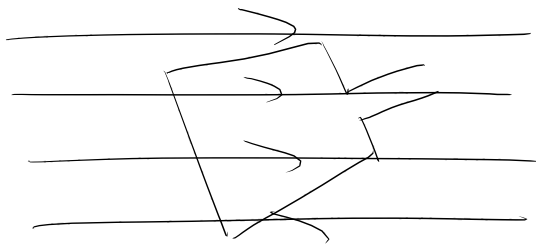
$$E = U_C + U_L = \frac{Q_0^2}{2C} = U_C(t=0)$$




$$\Phi_B = \vec{B} \cdot \vec{A} = BA \cos \Theta$$

$$\Theta(t) = \omega t + \delta$$

$$\Phi_B(t) = BA \cos(\omega t + \delta)$$

$$\mathcal{E} = - \frac{d\Phi_B}{dt} = \omega BA \sin(\omega t + \delta)$$


Example

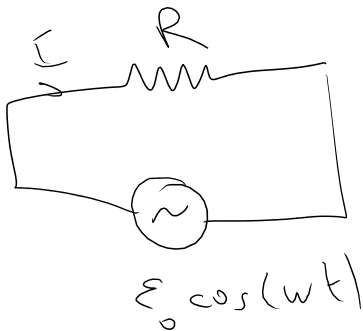

$$IR + \mathcal{E}_0 \cos(\omega t) = 0$$

$$I = - \frac{\mathcal{E}_0}{R} \cos(\omega t)$$

Example

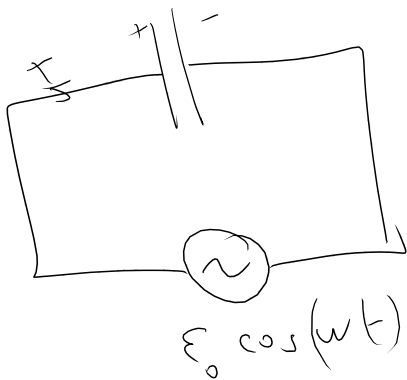

$$\frac{Q}{C} + \mathcal{E}_0 \cos \omega t = 0$$

$$Q = -\mathcal{E}_0 C \cos \omega t$$

$$I = \frac{dQ}{dt} = +\mathcal{E}_0 C \omega \sin \omega t$$


$$I = + \frac{\mathcal{E}_0}{\left(\frac{1}{\omega C}\right)} \sin \omega t$$

$$I_{\max} = \frac{\mathcal{E}_0}{\left(\frac{1}{\omega C}\right)} = \frac{\mathcal{E}_0}{X_C}$$

$X_C$ : capacitive impedance.

$$I = - \frac{\mathcal{E}_0}{\left(\frac{1}{\omega C}\right)} \cos\left(\omega t + \frac{\pi}{2}\right)$$

## Example

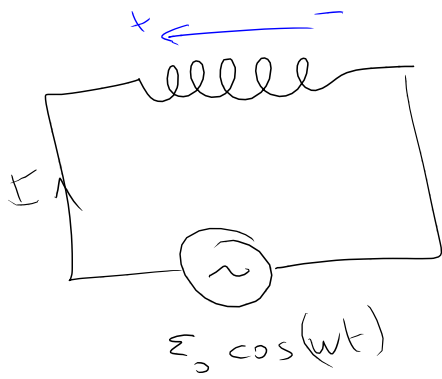

$$+L \frac{dI}{dt} + \epsilon_0 \cos \omega t = 0$$

assume  $\frac{dI}{dt} > 0$

$$\frac{dI}{dt} = -\frac{\epsilon_0 \cos \omega t}{L}$$

$$I = -\frac{\epsilon_0}{\omega L} \sin \omega t = -\frac{\epsilon_0}{X_L} \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$I_{\max} = \frac{\epsilon_0}{\omega L} \equiv \frac{\epsilon_0}{X_L}$$

$X_L = \omega L$  : inductive impedance

$$I \neq \frac{\epsilon}{X_L} \quad I_{\max} = \frac{\epsilon_{\max}}{X_L}$$

resistor

$$I = -\frac{\epsilon_0}{X_R} \cos(\omega t + 0)$$

$$X_R = R$$

capacitor


$$I = -\frac{\epsilon_0}{X_C} \cos\left(\omega t + \frac{\pi}{2}\right)$$


$$X_C = \frac{1}{\omega C}$$

inductor

$$I = -\frac{\epsilon_0}{X_L} \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$X_L = \omega L$$

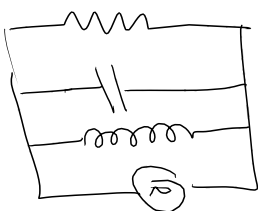

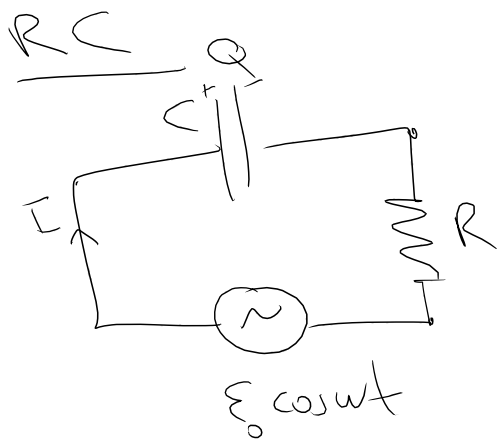

$$\frac{Q}{C} + IR = \varepsilon_0 \cos \omega t$$

$$I = \frac{dQ}{dt}$$

$$\frac{dQ}{dt} + \frac{Q}{RC} = \frac{\varepsilon_0}{R} \cos \omega t$$

$$Q = A \cos(\omega t + \delta)$$

$$-A\omega \sin(\omega t + \delta) + \frac{A \cos(\omega t + \delta)}{RC} = \frac{\varepsilon_0}{R} \cos(\omega t)$$

$$\sin(\omega t + \delta) = \sin \omega t \cos \delta + \cos \omega t \sin \delta$$

$$\cos(\omega t + \delta) = \dots$$

$$\omega t = 0 \quad -A\omega \sin \delta + \frac{A \cos \delta}{RC} = \frac{\varepsilon_0}{R}$$

$$\omega t = \frac{\pi}{2} \quad -A\omega \cos \delta - \frac{A \sin \delta}{RC} = 0$$

$$A = \frac{\varepsilon_0}{\sqrt{X_R^2 + X_C^2}} = \frac{\varepsilon_0}{Z}$$